

Experiment 5: Simple Resistor Circuits

Introduction

In this lab, we will investigate Ohm's Law, and study how resistors behave in various combinations. Along the way, you will establish that certain measurements are affected by the way in which circuit elements are connected to each other. In a direct current (DC) circuit, the relationship between the current (I) passing through a resistor, the potential difference (V) across the resistor, and the resistance (R) of the resistor is described by Ohm's Law:

$$V = IR \quad (1)$$

In Part 1 of the experiment, we will verify this law by measuring the potential difference (i.e. voltage drop) across resistors in series and parallel. The typical resistor used here is a carbon resistor that is usually marked with colored bands to indicate its resistance in Ohms, as seen in Figure 1 (see Lab 2 for more detail). In Part 2, we will proceed to investigate how resistors behave in various combinations. To help us, we introduce two additional circuit laws:

Kirchhoff's First Law - The current entering a junction is equal to the current leaving a junction.

Kirchhoff's Second Law - The sum of all the voltage drops around a closed circuit is zero.



Figure 1: Resistor color codes: Black=0, Brown=1, Red=2, Orange=3, Yellow=4, Green=5, Blue=6, Violet=7, Gray=8, White=9.

We first consider N resistors in *series* as shown in Figure 2. Since there are no branching junctions in the circuit, the current entering through all the resistors is identical, i.e. $I = I_1 = I_2 = I_3 = \dots = I_N$. We also know from Kirchhoff's Second Law that $V = V_1 + V_2 + V_3$

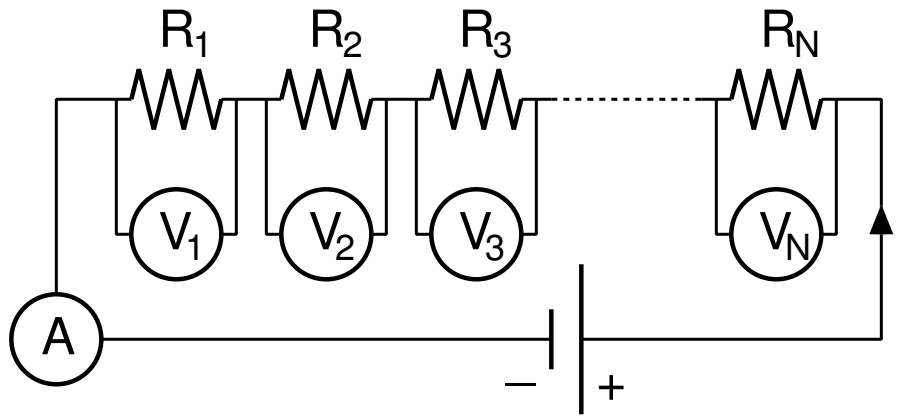


Figure 2: Resistors in series.

For a parallel arrangement, all the resistors have the same potential difference (since they are essentially connected to the "same" two points). Thus $V_1 = V_2 = V_3 = \dots = V_N$. Since $I = V/R$ (from Ohm's Law), we can write Equation 3 as

$$\frac{V}{R} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots + \frac{V_n}{R_n}$$

(your first resistor). Setting the power supply to 10 V, measure the current in the circuit, and the potential difference across R_1 . Record this as V_1 . Move the Voltmeter to measure the potential difference across R_2 and R_3 . Now find the total potential difference across all three resistors. Record this as V and verify that $V = V_1 + V_2 + V_3$. Discuss the following questions in the analysis section of your lab report:

1. Find the experimental value of the resistance of each resistor using Equation 1 (i.e. $R_1 = V_1/I$, etc.).
2. Find the experimental value of the total effective resistance R in series using the value of I , total V , and Equation 3.
3. Compare resistance values for R_1 , R_2 , and R_3 obtained from the ohmmeter with those found using Ohm's Law.
4. (Why didn't we use resistor number 4?!?) Using the measured values of resistance, estimate the value of I with all 4 resistors in series ($v=10V$), and compare the result to the resolution of the Ammeter on it's most sensitive scale.

Procedure 1B - Resistors in Parallel:

Construct a parallel circuit as shown in Figure 3 using **ALL**

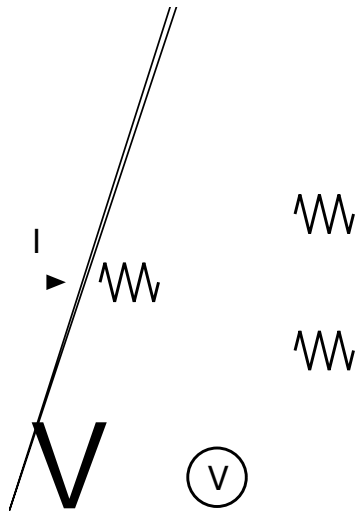


Figure 4: Resistors in series-parallel combination.